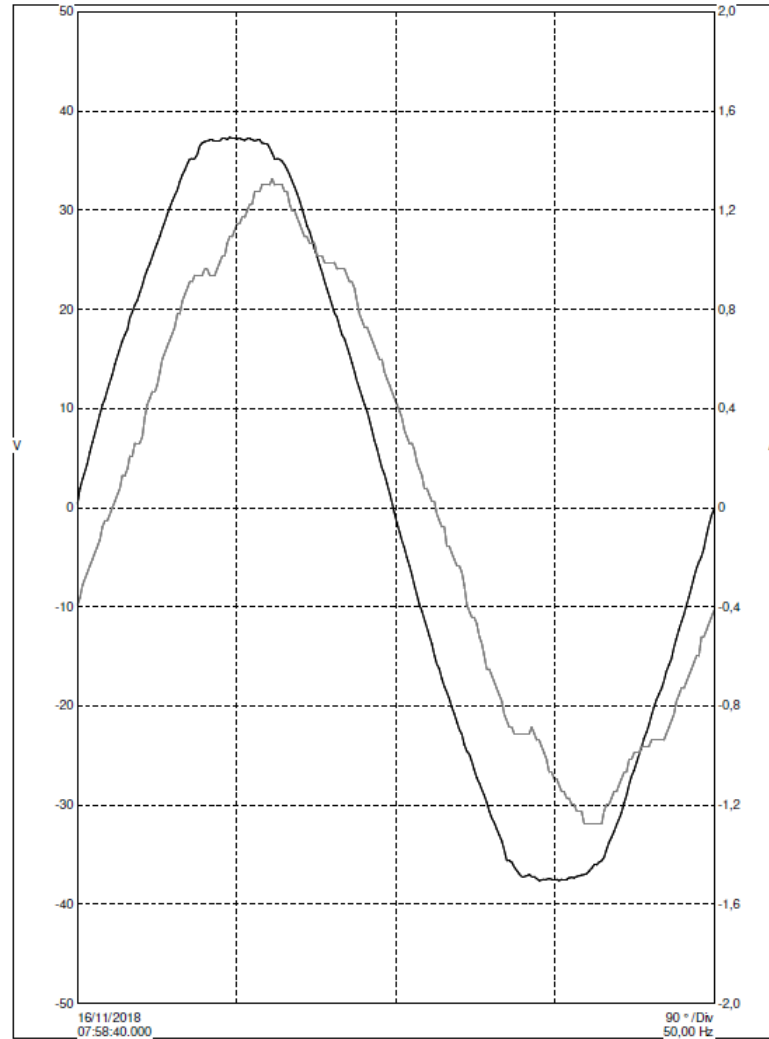
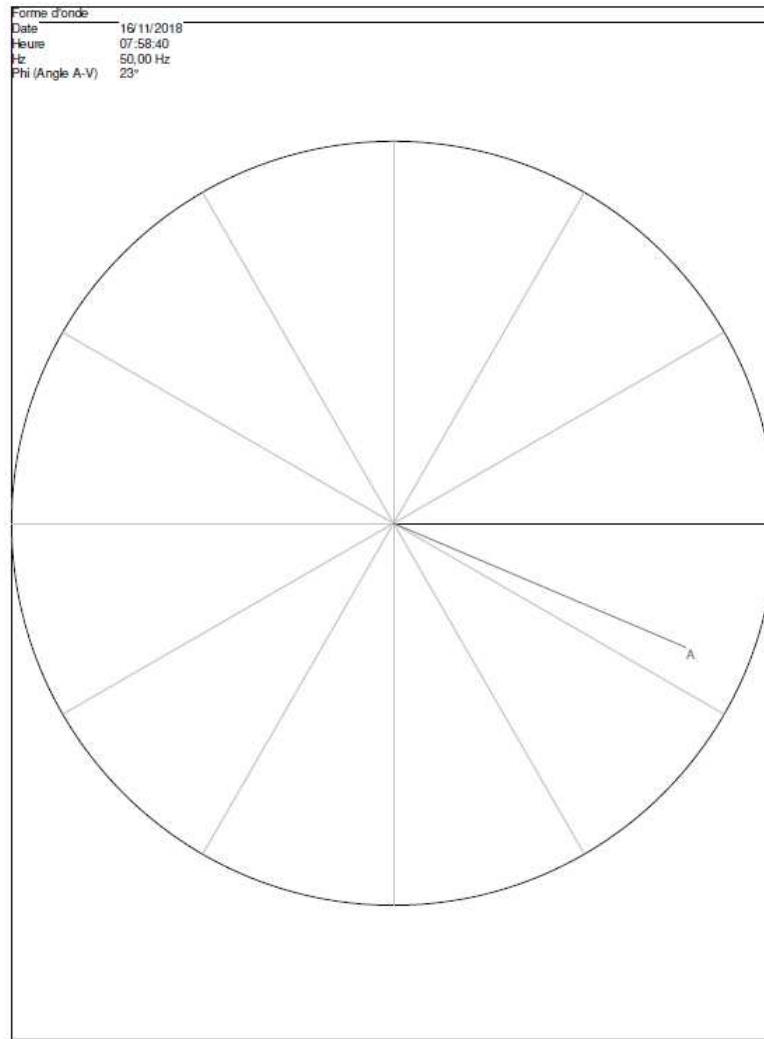


# Circuit RL avec condensateurs

V RMS - 26,9 V Peak- - 37,6 V Peak+ - 37,3 V  
 A RMS - 0,9 A Peak- - 1,3 A Peak+ - 1,3 A



V<sub>hi</sub> - 26,8 V  
 A<sub>hi</sub> - 0,8 A



Date	Heure	Voie	W	WDC	var	VA	PF	DPF
16/11/2018	07:58:40	Monophasé	21,3	-0,0	8,4	22,9	0,930	0,931