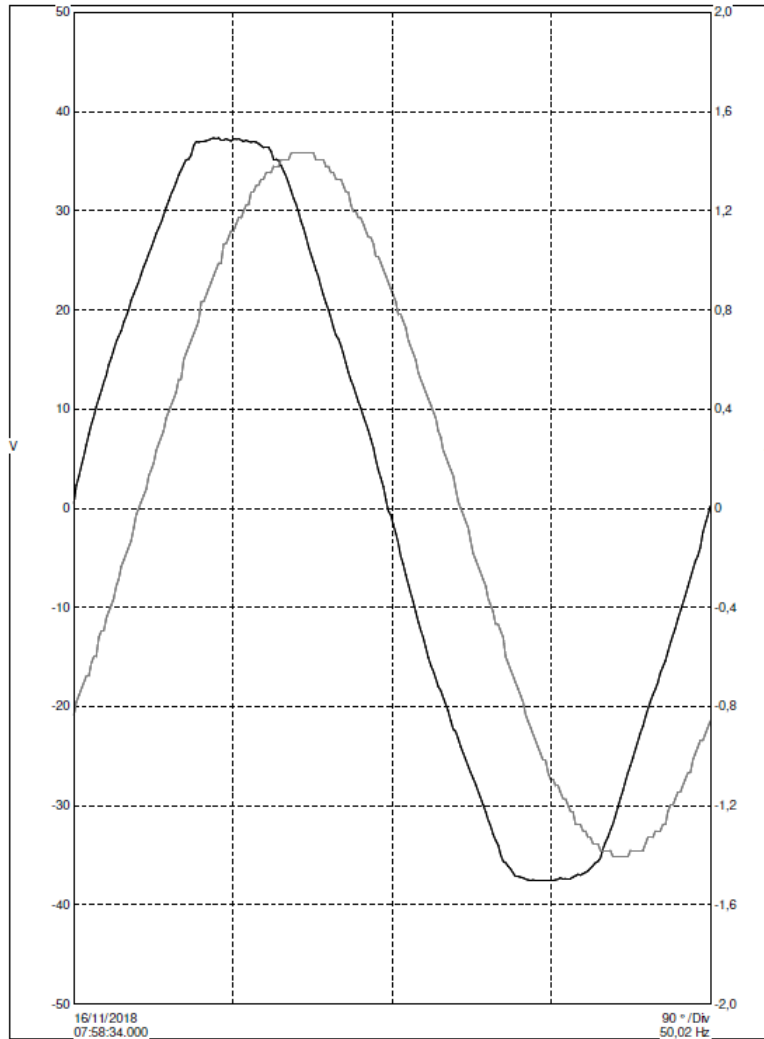
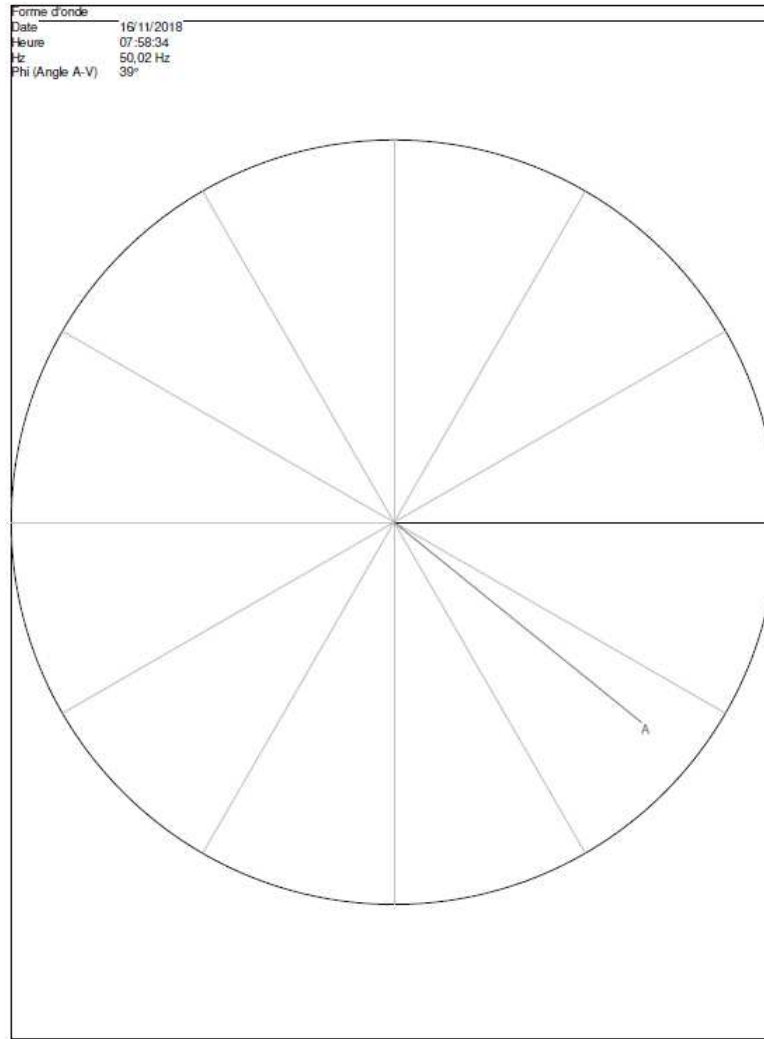


# Circuit RL sans condensateurs

V RMS 26,9 V Peak - -37,5 V Peak+ +37,3 V  
 A RMS 1,0 A Peak - -1,4 A Peak+ +1,4 A



Vh1 26,9 V  
 Ah1 1,0 A



Forme d'onde  
 Date 16/11/2018  
 Heure 07:58:34  
 Hz 50,02 Hz  
 Phi (Angle A-V) 39°

Date	Heure	Voie	W	WDC	var	VA	PF	DPF
16/11/2018	07:58:34	Monophasé	20,4	-0,0	17,1	26,6	0,766	0,767